



Chapter 9


Discrete Control Using Programmable Logic Controllers



Chapter 9: Discrete Control

Sections:

1. Discrete Process Control
2. Ladder Logic Diagrams
3. Programmable Logic Controllers

 



Sec 9.1: Discrete Process Control

- **Continuous Control**: deals with controlling continuous variables or parameters in the system.
- **Discrete Control**: Control systems that operate on parameters and variables that change at **discrete moments in time** or at **discrete events**,
 - usually binary (0 or 1, off or on, open or closed, etc.)
 - Called also: **switching systems**.



Sensors and Actuators Used in Discrete Process Control

Sensors	Interpretation	Actuators	Interpretation
Limit switch	Contact/no contact	Motor	On/off
Photo-detector	On/off	Valve	Open/closed
Timer	On/off	Clutch	Engaged/not engaged
Push-button switch	On/off	Control relay	Contact/no contact
Control relay	Contact/no contact	Light	On/off
Circuit breaker	Contact/no contact	Solenoid	Energized/not energized



Categories of Discrete Control


- **Logic control:** event-driven changes
- **Sequencing:** time-driven changes

- **Logic Control:** a switching system whose output at any moment is determined exclusively by the values of inputs.
 - No memory
 - No operating characteristics that depend on time
 - Also called *combinational logic control*



Logic control example: Die stamping process

 - When the master switch is turned on the die-stamping piston is to reciprocate between the extended and retracted positions, stamping parts that have been placed in the machine.





Elements of Logic Control

- Logic gates:




AND: output = 1 if all inputs = 1, zero otherwise

OR: output = 1 if any input = 1, zero otherwise

NOT: output = 1 if (single) input = 0, and vice versa

NAND: combination of AND and NOT

NOR: combination of OR and NOT

   




Boolean Algebra & Truth Tables


AND function is expressed as

$$Y = X1 \cdot X2$$

 


OR function is expressed as

$$Y = X1 + X2$$

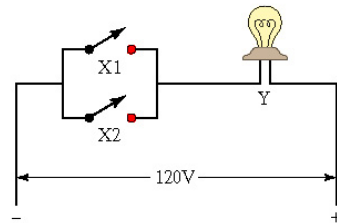

NOT function is expressed as

$$Y = \overline{X1}$$

 

Inputs		Output
X1	X2	$Y = X1 \cdot X2$
0	0	0
0	1	0
1	0	0
1	1	1

Inputs		Output
X1	X2	$Y = X1 + X2$
0	0	0
0	1	1
1	0	1
1	1	1

Inputs	Output
X1	$Y = \overline{X1}$
0	1
1	0



NAND and NOR Functions

(a) NAND





<i>Inputs</i>		<i>Output</i>
X1	X2	$Y = \overline{X1 \cdot X2}$
0	0	1
0	1	1
1	0	1
1	1	0

(b) NOR

<i>Inputs</i>		<i>Output</i>
X1	X2	$Y = \overline{X1 + X2}$
0	0	1
0	1	0
1	0	0
1	1	0



Symbols for Logical Gates

    	U.S. symbol	ISO symbol
AND		
OR		
NOT		
NAND		
NOR		



Example 1:

- On a particular piece of operator-controlled production equipment, the production process may only be performed by the operator activating two safety switches, located at some distance from each other. This is to prevent the equipment from accidentally starting whilst the operator is loading or unloading the machine. The switches have to be depressed together by the operator using both hands.
- (a) What is the truth table for this operation?
- (b) What is the Boolean logic expression for this operation?
- (c) What is the **logic network diagram** for the operation?




Example 1 solution:


- (a) Where X1 is first switch, and X2 is second switch, and Y is the output of switch activation.

Inputs		Output
X1	X2	Y
0	0	0
0	1	0
1	0	0
1	1	1

- (b) $Y = X1 * X2$
- (c)

 

logic network diagram


 




  Example 2:

Write the Boolean logic expression for the pushbutton switch system below using the following symbols:


X1 = START, X2 = STOP, Y1 = MOTOR, and Y2 = POWER-TO-MOTOR.



logic network diagram



Example 2 solution:

 

Truth Table

<i>Start</i>	<i>Stop</i>	<i>Motor</i>	<i>Power-to-Motor</i>
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	0
0	0	1	1
0	1	1	0
1	0	1	1
1	1	1	0



Sequencing



A switching system that uses **internal timing devices** to determine when to initiate changes in output variables

- Examples: **Washing machines, dryers, dishwashers, Traffic light.**




Sequencing

- Outputs are usually generated “open loop”
 - No feedback that control function is executed
- Sequence of output signals is usually cyclical, as in a high production work cycle
 - The signals occur in the same repeated pattern within each regular cycle
- Common sequencing devices:
 - **Timer** – output switches on/off at preset times
 - **Counter** – counts electrical pulses and stores them



Sec 9.2: Ladder Logic Diagrams

 
- Another way for drawing Logic Network Diagrams.
- A diagram where logic elements are displayed along horizontal lines (rungs) connecting two rails.
- Combines both: logic and sequencing control.






Ladder Logic Diagrams



 
- Components of Ladder Diagrams:
 1. **Contacts** - logical inputs, e.g., limit switches, photo-detector.
 2. **Loads (coils)** - outputs, e.g., motors, lights, alarms, solenoids.
 3. **Timers** - to specify length of delay.
 4. **Counters** - to count pulses received





Components of Ladder Logic Diagram


 


   Ladder symbol	Hardware component
(a) 	Normally open contacts (switch, relay, other ON/OFF devices)
(b) 	Normally closed contacts (switch, relay, etc.)
(c) 	Output loads (motor, lamp, solenoid, alarm, etc.)
(d) 	Timer
(e) 	Counter



Example 1



- Construct the ladder logic diagrams for the **AND** gate.
- Solution:**

  



Example 2



- Construct the ladder logic diagrams for the **OR** gate.
- Solution:**

  



Example 3

- Construct the ladder logic diagrams for the **NOT** gate.
- Solution:**

  




Example 4

- Construct the ladder logic diagrams for the **NAND** gate.
- Solution:**

(a) NAND		
Inputs		Output
X1	X2	$Y = \overline{X1 \cdot X2}$
0	0	1
0	1	1
1	0	1
1	1	0

 


- If X1 or X2 remain open then C coil is unexcited and C contact remains closed, therefore Y is on.
- If X1 and X2 are closed then C coil is excited and C contact is opened and Y is off



Example 5

- Construct the ladder logic diagrams for the **NOR** gate.
- Solution:**

(b) NOR		
Inputs		Output
X1	X2	$Y = \overline{X1 + X2}$
0	0	1
0	1	0
1	0	0
1	1	0


 


- If X1 and X2 remain open then C coil is unexcited and C contact remains closed, therefore Y is on.
- If X1 or X2 are closed then C coil is excited and C contact is opened and Y is off



Example 6: Safety switches



- The production process may only be performed when the operator activates two spring activated safety switches. The switches have to be depressed and held closed together by the operator using both hands.

  



  
Example 7: Push Button

- Create ladder logic diagram for Push Button switch.



$(X1 \text{ OR } Y1) \text{ AND } (\text{NOT } X2)$

$$(X1 + Y1) \cdot \overline{X2}$$

 


Latched circuit



Example 8:


- A motor controlled by stop and start push button switches.
- One signal light must be illuminated when the power is applied to the motor and another when it is not applied.

 





Example 9.6 (textbook): Tank Filling

- **X1**: start the process
- **S1** and **S2**: Solenoid valves
- **C1** & **C2**: Control relay for S1 and S2
- **FS**: Float Switch
- When the tank is full ($FS = 1$), a timing process (**T1**) of 120 sec will be started
- valve 2 start to dump fluid for 90s and stop the process

 





Example 9.6 (textbook): Tank Filling

  




Example 9.6 (textbook): Tank Filling

  




Latched Output

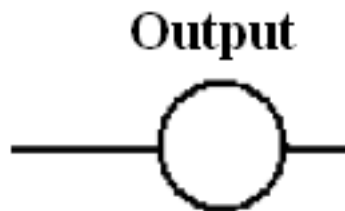
- Used to keep an output on until a stop action occurs.



On/off output

 

 
Latched output: stays on until
stopped by other rung




Un-latch output: stops latched
outputs



Latched output: Example

 


Can be replaced by

 




 
Exercise: Die stamping process

- When the master switch is turned on the die-stamping piston is to reciprocate between the extended and retracted positions, stamping parts that have been placed in the machine.






Exercise: Die stamping process

  




Sec 9.3: Programmable Logic Controller (PLC)

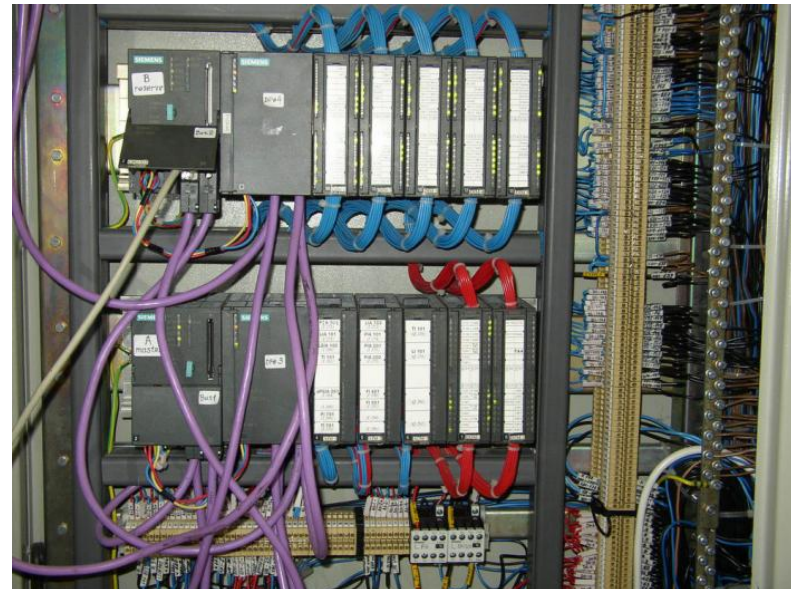- A **microcomputer-based controller** that uses **stored instructions** in programmable memory to implement logic, sequencing, timing, counting, and arithmetic functions through digital or analog modules, for controlling machines and processes.





Components of a PLC

 



Advantages of PLCs Compared to Relay Control Panels

- Programming a PLC is easier than wiring a relay control panel
- PLC can be reprogrammed
- PLCs take less floor space
- Greater reliability, easier maintenance
- PLC can be connected to computer systems (CIM)
- PLCs can perform a greater variety of control functions



Typical PLC Operating Cycle

1. **Input scan** – inputs are read by processor and stored in memory
2. **Program scan** – control program is executed
 - Input values stored in memory are used in the control logic calculations to determine values of outputs
3. **Output scan** – output values are updated to agree with calculated values
 - Time to perform the three steps (scan time) varies between 1 and 25 msec



PLC Programming

- Graphical languages:
 1. Ladder logic diagrams – most widely used
 2. Function block diagrams – instructions composed of operation blocks that transform input signals
 3. Sequential function charts – series of steps and transitions from one state to the next (Europe)
- Text-based languages:
 1. Instruction list - low-level computer language
 2. Structured text – high-level computer language



PLC Programming

